

ECEE 434 Lab 1 - Mosfet Inverter

Liz MacLean & Carl Anderson

October 13, 2017

Contents

Introduction & Background	2
Procedure	3
Results	8
Conclusion	13

Introduction & Background

This lab provide an introduction to an IC chip creation software called Cadence Virtuoso. Virtuoso is software that allows one to create and simulate analog circuit designs. In this particular instance, the goal was to learn Virtuoso's design environment by creating a simple CMOS inverter circuit. Then simulate its output when applied to a semi-real world situation (load capacitor to simulate chained inverters, or other output loads).



Procedure

For the first portion of the experiment, an NMOS transistor circuit (Fig. 1) was put under DC analysis at a gate-source voltage of 5V.

After collection a single I-V curve from this transistor, the next test was to vary V_{GS} from 1 to 5V by 0.5V steps. This would result in a *family* of I-V curves to be plotted when tested under a parametric analysis.

Once a single I-V curve and the family of I-V curves were plotted for the NMOS transistor, the same analyses were run for a PMOS transistor, as seen in Fig. 2.

It should be noted that the PMOS transistor have flipped polarities, thus V_{DD} (V1) is connected to the bottom of the transistor, and ground is connected to the top.

The second part of the experiment was to demonstrate the concept of hierarchy in circuit design and simulation. For this portion, a NMOS and PMOS transistor were connected, and symbolic pins were added for outside connections. This was then saved as a cell under the name “inverter” (Fig. 3). This is the equivalent to making a function in a coding language.

Once the inverter cell was created, it was added to the ECEE 434 component library. This component was then used in another circuit, where each of the pins that had been added to the initial cell (vdd, in, out, gnd) were connected to actual components that would complete the circuit and make it functional. Figure 4 is the resultant circuit.

The circuit was then put under transient analysis to see the input and output voltages over the duration of 1 microsecond.



 


Figure 1: NMOS Circuit Schematic with $V_{GS} = 5\text{V}$ and $V_{DD} = 5\text{V}$



 


Figure 2: PMOS Circuit Schematic with $V_{SG} = 5V$ and $V_{DD} = 5V$



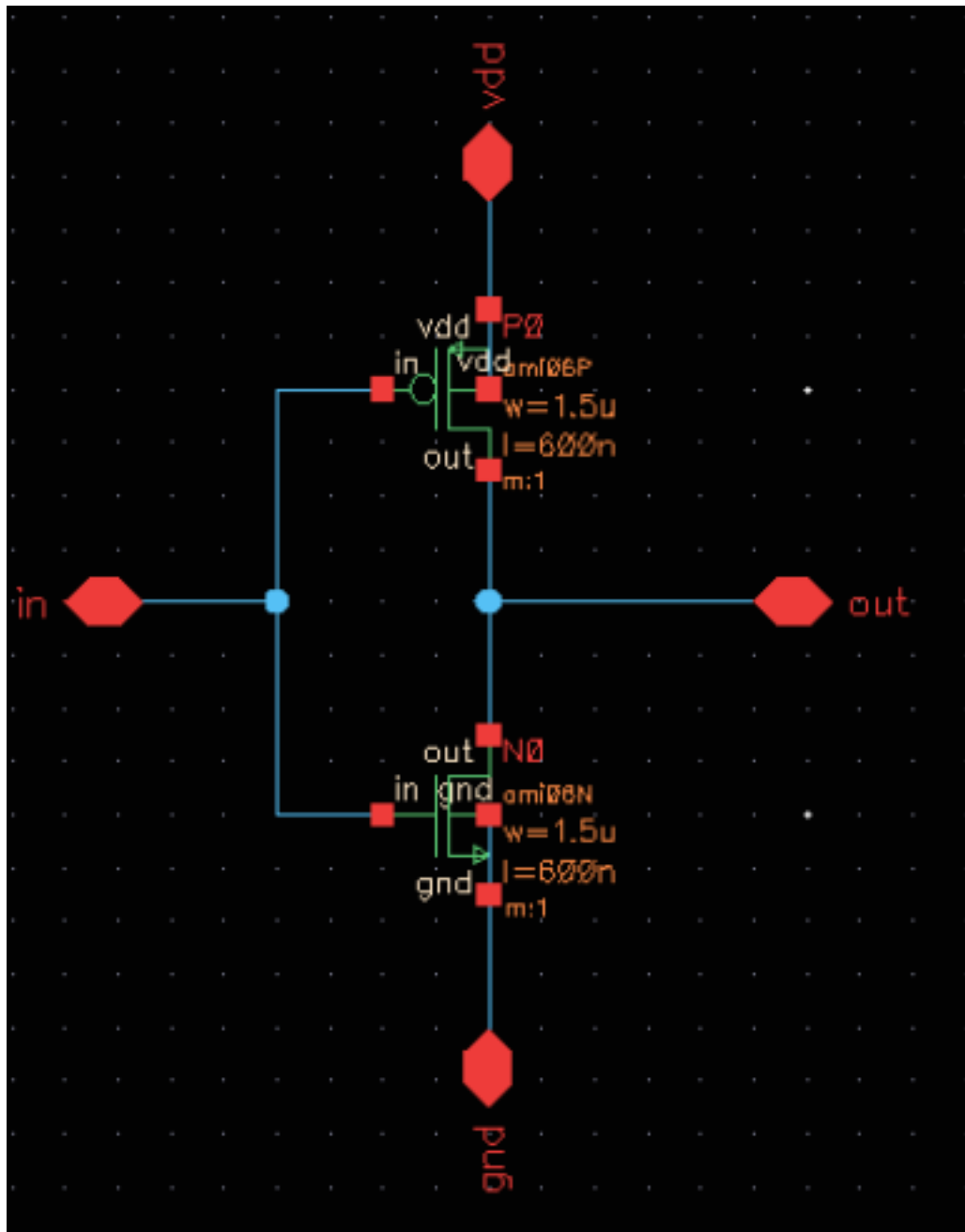


Figure 3: Inverter Circuit



 


Figure 4: Complete Schematic with Imported Inverter Component



Results

The result of the DC analysis for the NMOS and PMOS were simple I-V curves (Fig. 5 and 6) that plotted the drain current, i_D versus the drain to source voltage, V_{DS} . When comparing the NMOS simple I-V curve to that of the PMOS, the difference in shape of the curves despite having equivalent values should be noted. The NMOS' curve rises more quickly than that of the PMOS, and also stabilizes moreso, whereas the PMOS curve still rises past the threshold voltage is reached.

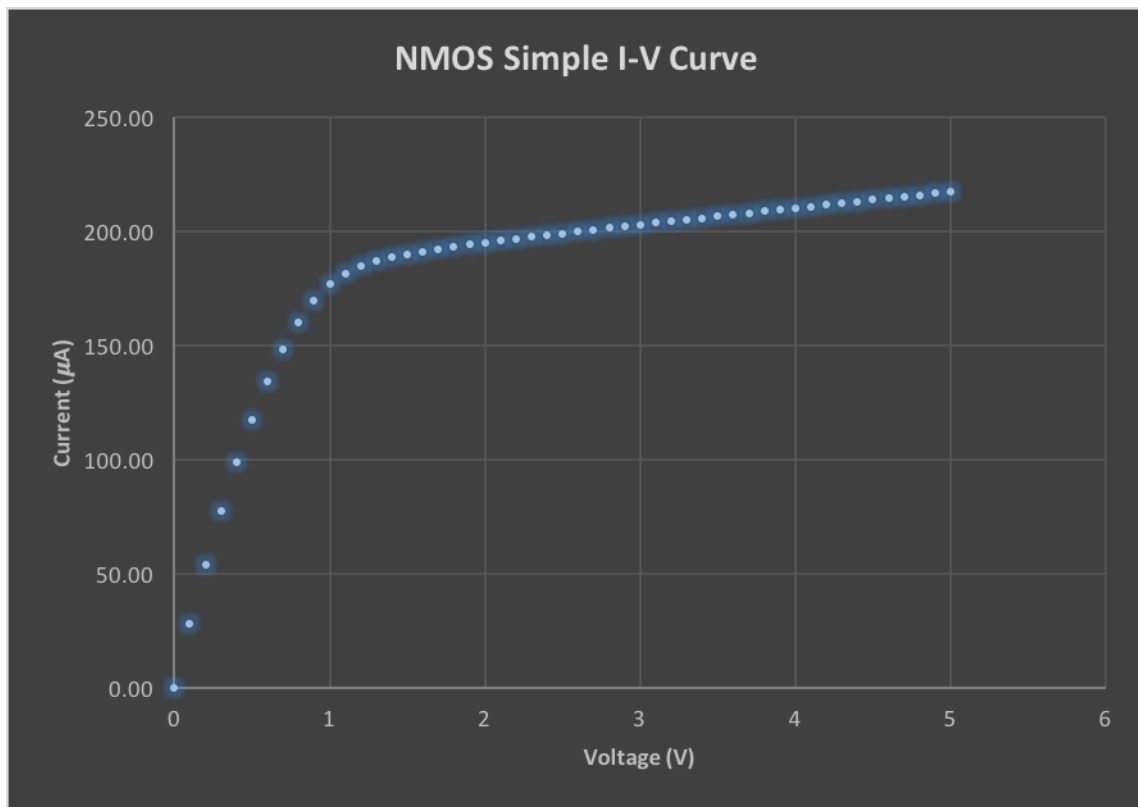


Figure 5: NMOS Simple I-V Curve

When the transistors were placed under parametric analysis (Fig. 7 and 8) for a multitude of V_{GS} values, it is even more evident that the PMOS transistor's current evens out slower than that of the NMOS. This information is relevant because it explains the design preference of NMOS over PMOS transistors when designing a circuit, as the NMOS is faster due to the carriers being electrons as opposed to holes. In addition, it is important to realize their differences in behavior for when they are combine in components such as CMOS transistors.

For the second part of the experiment, where a transient analysis was run on the inverter circuit, as expected, the input voltage of the circuit was successfully inverted, as seen in Figure 9.



 


Figure 6: PMOS Simple I-V Curve

 


Figure 7: NMOS Family I-V Curve



 


Figure 8: PMOS Family I-V Curve



 


Figure 9: Transient Analysis of Inverter



While the input is perfectly square, as chosen when making the circuit, the output voltage has curved rising and falling edges. This is due to the nature of NMOS and PMOS components. Although there is a clear point at which the voltage switches the behavior of the transistor from open to closed and vice-versa, there is still a time of adjustment before the transistor reaches true saturation, thus the rounded edges.



Conclusion

The simulation of the inverter circuit with load capacitor showed what a real world application would look like for a CMOS inverter. Due to capacitances in the devices themselves, the response of the circuits is not an instant transition from high to low (or vice versa) as discovered in theoretical designs. Capacitance and resistance inherent in the manufacture of these devices alter the response times in a mostly predictable way that needs to be accounted for. Further, the lab procedure provided an introduction to the schematic capture, library construction, and simulation aspects of Virtuoso.

This lab provided a two fold introduction to digital electronics and design.

