

ECEE 434 Lab #5 - Positive/Negative Flip-flop

Liz MacLean & Carl Anderson

November 17, 2017

Contents

Introduction & Background	2
Procedure	3
Results	4
Conclusion	5

Introduction & Background

The previous experiment introduced the use of D-latches, how they operate, and their limitations. This experiment introduces a different kind of latch called a flip-flop. A flip-flop differs from a latch in that it registers data while the clock is rising, rather than when it is high. A negative version can also be created.

The purpose of this experiment is to build a positive flip-flop and characterize it. The D-latch from the previous experiment is used in this one to create the new circuit.



Procedure

In order to achieve the objective of this experiment, the following procedure was followed:

- Build a negative latch and show its functionality.
 - Use the latch circuit from the previous experiment
 - Simulate its output using Spectre and show the graph.
- Build a positive flip-flop and show it's functionality
- Using the definitions of hold time and setup time for flip-flops, characterize the flip-flop using those measurements.



Results

some stuff resulted in more stuff.



Conclusion

Some cool stuff happened.

