

ECEE 434 Lab #5 - Positive/Negative Flip-flop

Liz MacLean & Carl Anderson

November 30, 2017

Contents

Introduction & Background	2
Procedure	3
Results	4
Conclusion	6

Introduction & Background

The previous experiment introduced the use of D-latches, how they operate, and their limitations. This experiment introduces a different kind of latch called a flip-flop. A flip-flop differs from a latch in that it registers data while the clock is rising, rather than when it is high. A negative version can also be created.

The purpose of this experiment is to build a positive flip-flop and characterize it. The D-latch from the previous experiment, and a negative D-latch, is used in this one to create the new circuit.

In order to characterize the positive flip-flop two specific measurements will be considered. The first is “setup-time.” Setup-time is defined as the minimum amount of time before the clock’s leading edge that the data must be stable for it to be latched correctly. Data that is switched in violation of the setup-time parameter will not have time to propagate through the circuit.

The second parameter is called “hold-time.” Hold-time is defined as the minimum amount of time after the clock’s leading edge during which the data must be stable. The effect is similar to the setup-time.



Procedure

In order to successfully create a positive D flip-flop that saved data on the rising edge of the clock, two D-latches, one negative and one positive had to be combined. The positive D-latch was created in the previous lab, and the negative D-latch was essentially the same, except that there was an additional inverter used. Then, these two components were connected in series, and the outputs from both latches were recorded. The output of the second latch (and thus the output of the combination of the two) is expected to have the behavior of a positive D flip-flop. The hold and setup times were then measured by measuring the time between when the clock changed, and the data line rose or fell.



Results

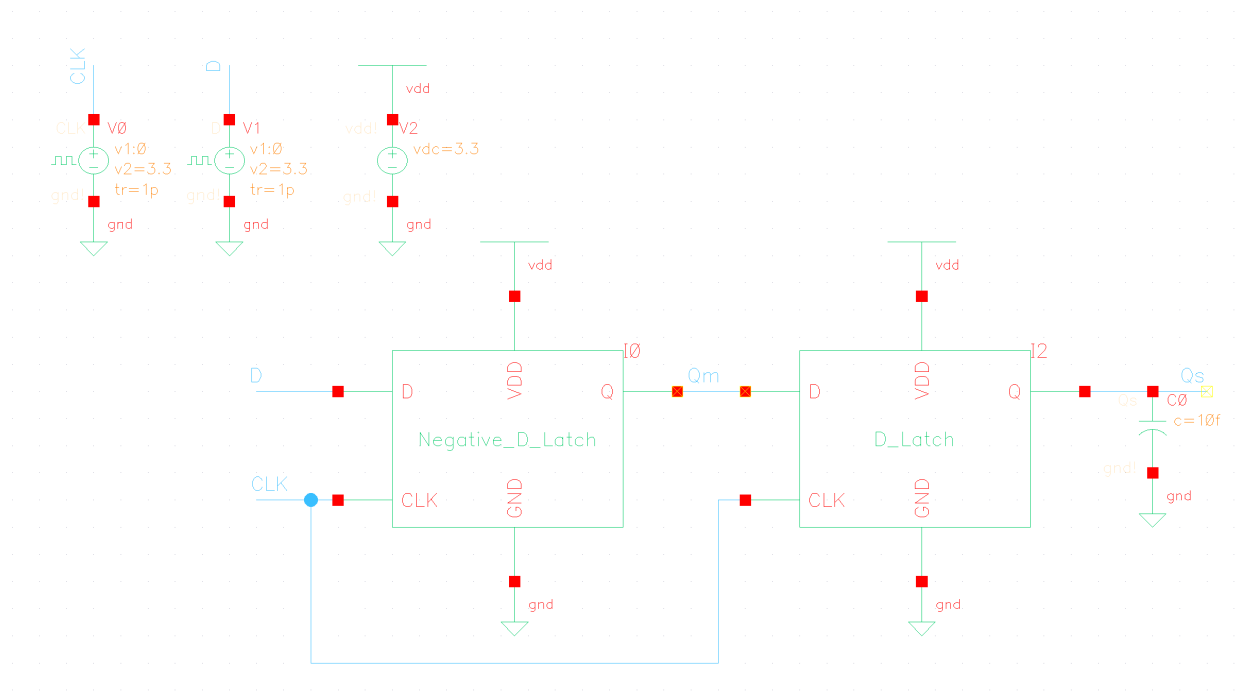


Figure 1: Schematic used for Positive Flip-flop

The overall circuit can be seen in Fig. 1. Before this circuit was built, first a negative latch was created using the D-latch from the previous experiment. However, the difference from previous was the addition of an inverter to the input of the D-latch within the circuit. This is not seen in the schematic, because it was built in to the symbol. The operation of the Negative D-latch can be seen in Fig. 2 on the Qm graph. Only when the clock is negative will the data be accepted into the circuit, which is reflected in the output plot.

Further, the operation of the D-flip-flop can be seen at the Qs output. The output data changes only on the leading edge of the input clock. Otherwise, the output is constant.

The setup and hold times were found as follows, using the methods mentioned in the procedure:

$$setuptime = 0.521ns$$

$$holdtime = 0.547ns$$



 


Figure 2: Output plot of Positive Flip-flop. CLK, D, Qm, Qs, shown (listed as shown from top to bottom).



Conclusion

Overall, the results were correct with respect to initial behavioral assumptions. For the negative latch, the output data, Q_m , only changed when the clock was negative, and the output data of the entire schematic, Q_s , only changed on the rising edge of the clock. Not only did this exercise with latches assist with a deeper understanding of how latches work, but it also established a clear difference between latches and flip flops through interactive methods. In the future, it would be interesting to create a negative D flip-flop, as well as play with the order of the latches by placing them in parallel, or in opposite series from this example. This experiment is also useful because it starts to introduce students to ways to manipulate signals as desired. For example, if a device uses chip select for certain functionality, and the user wants to access each of these functionalities at different times, a flip flop may be a useful way to change this data line. It is also important to appreciate the measuring of the setup and hold times, because without those values being known, a student may erroneously try to change the data line too soon, or do some other change that will corrupt the stored data. With these values, measures can be taken to prevent future invalid or incorrect outputs.

