

ECEE 434 Lab #3 - Logic Gates

Liz MacLean & Carl Anderson

October 27, 2017

Contents

Introduction & Background	2
Procedure	3
Results	4
Conclusion	5

Introduction & Background



Procedure

The goal of this lab is to have the rising and falling propagation delays be equivalent. Since we are adjusting the size of the transistors for this design requirement to be true, the most straightforward way of calculating them is using the propagation time equations.

$$t_{PHL} = 0.69 * R_n * C_{load}$$

$$t_{PLH} = 0.69 * R_p * C_{load}$$

Based off of these equations, the only unknowns are the resistance values for the transistors, R_N and R_P .

$$R_N = \frac{12.5}{(W/L)_n}$$

$$R_P = \frac{30}{(W/L)_p}$$

After setting R_n equal to R_p so that the t_{PLH} and t_{PHL} values would be equivalent, the ratio of p to n was:
 $p = 2.4n$

Since the default width for the transistors in Cadence is $1.5\mu m$, that value was chosen for the n-type transistor, and then p was calculated to be $3.6\mu m$.



Results



Conclusion

