

ECEE 434 Lab #4 - D-latch

Liz MacLean & Carl Anderson

November 17, 2017

Contents

Introduction & Background	2
Procedure	3
Results	4
Conclusion	6

Introduction & Background

A D-latch circuit is a combination circuit consisting of CMOS inverters, transmission gates, and a clock signal. This circuit will transmit the signal on the D input line to the Q output when the CLK signal is high. This is useful in the case of noise, as it results in short changes to the input to not affect the output. In addition, D-latches are used for storing states, specifically when the clock is low. Storing the state can be useful when using chip select on a specific chip that is used for multiple things.



Results

For the initial reading of the D-Latch data, where no failure was expected, the input of the clock, clk, as well as the data line, D, resulted in a correct reading for the output, Q (Fig. 2). As anticipated, when the clock and the data line were high, so was the input, and when the clock was low, no matter the data line, the output Q remained what it was when the clock was high.

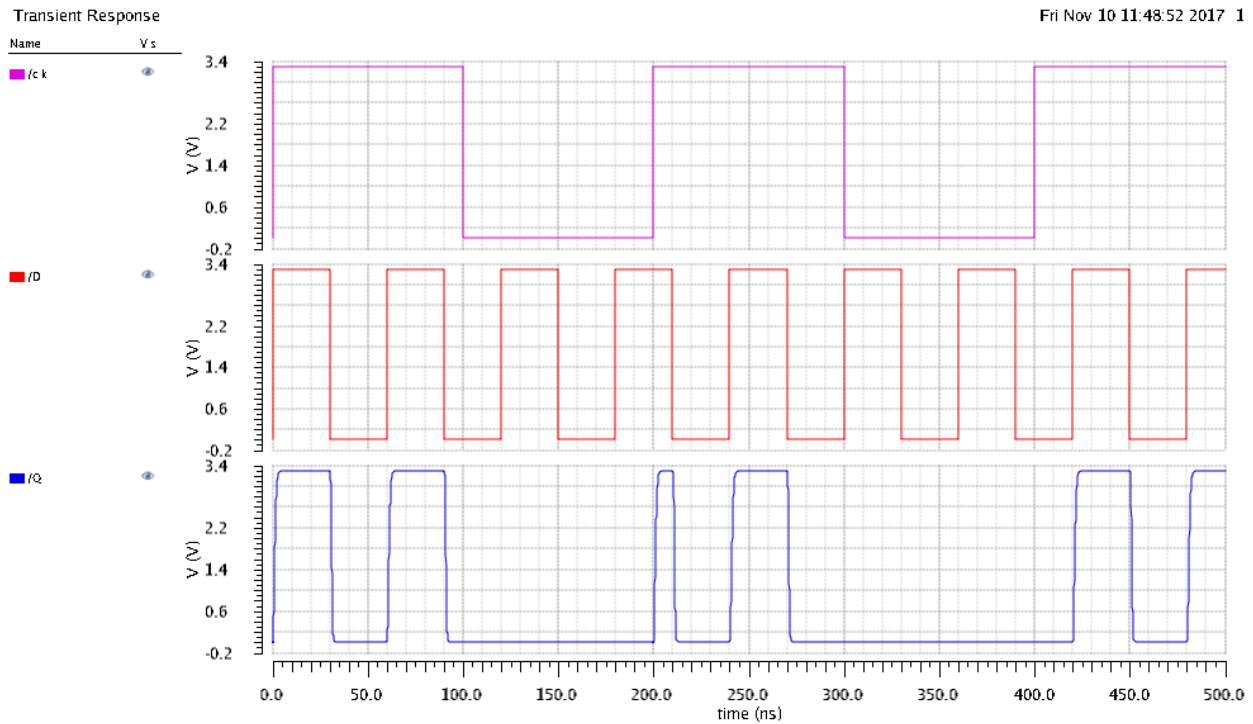


Figure 2: Correct Simulated Output from a D-Latch Circuit

When the frequency was high enough, it broke the behavior of the D-Latch. This frequency is related to the t_p of the circuit. When the frequency of the circuit exceeds the t_p , the transitions don't have enough time to fully change. In the original graph, t_p was observed to be roughly 3ns, so the CLK was adjusted to have a 3ns period with a 50% duty cycle (1.5ns PW). The frequency at that rate was $\frac{1}{3ns} = 333.333MHz$.





Figure 3: Broken Simulated Output from D-Latch Circuit



Conclusion

The purpose of this experiment was not only to understand the functionality of the D-Latch, but to also understand the limitations of it. If this flip-flop were to be used in the field, knowing that it has a maximum frequency, and not going over that will be very helpful in the design of the circuit and the components surrounding it. In addition, seeing the digital output is very different from simply looking at a truth table, and gives a deeper comprehension to how circuits like the D-Latch work.

